

ASSIGNMENT

M Sai Santhosh Kumar

santhoshmandarapu1221@gmail.com

IITH - Future Wireless Communications (FWC)

CONTENTS

1	Question	1
2	Components	1
3	Truth Table	1
4	Excitation Table	1
5	Truth table for next 3 stages	1
6	next 3 stages	1
7	Hardware	2
8	Implementation	2

1 QUESTION

Consider a 3 bit counter, designed using T flip-flops, as shown below: Assuming the initial state of

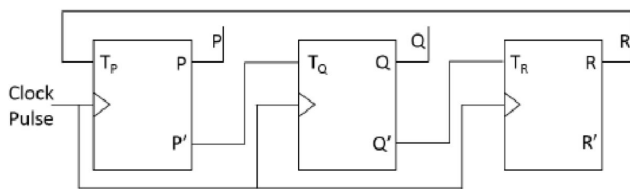


Fig. 1

the counter given by PQR as 000, what are the next three states?

2 COMPONENTS

Component	values	Quantity
Arduino	UNO	1
Jumperwires	M-M	35
Breadboard		2
LED		3
Resistor	220ohms	3
IC	7476	3

Figure.a

3 TRUTH TABLE

T	Q	Q'
0	Q	Q'
1	Q'	Q

Truth table for "T" flipflop

4 EXCITATION TABLE

Q	Qn	T
0	0	0
0	1	1
1	0	1
1	1	0

Excitation table of T- flipflop

5 TRUTH TABLE FOR NEXT 3 STAGES

P	Q	R	P+	Q+	R+
0	0	0	0	1	1
0	1	1	1	0	1
1	0	1	0	0	0

Figure :b

6 NEXT 3 STAGES

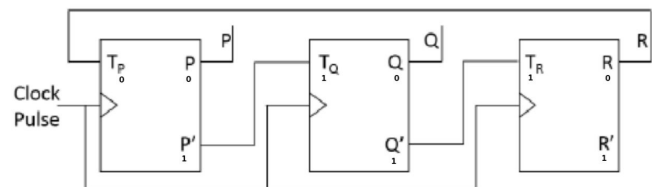


Fig. 2

