

ASSIGNMENT

M Sai Santhosh Kumar
santhoshmandarapu1221@gmail.com
IITH - Future Wireless Communications (FWC)

27-03-2023

Contents

1	Question	2
2	Components	2
3	TruthTable	3
4	ExcitationTable	3
5	Truthtable(3-stages)	3
6	3stages	4
7	Hardware	5
8	Implementation	5
9	Procedure	6

1 Question

Consider a 3 bit counter,designed using T flip-flops,as shown below: Assuming

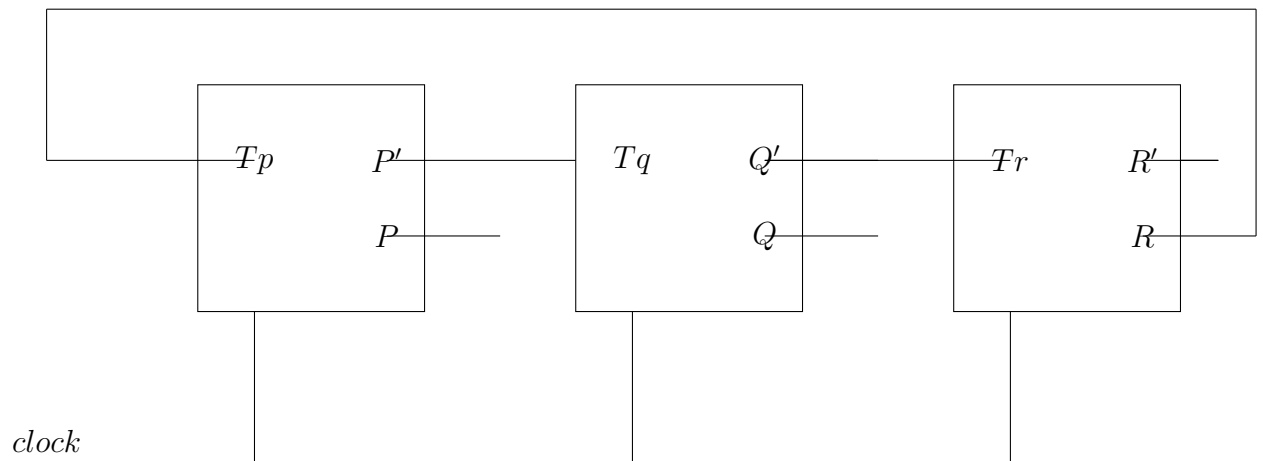


Figure 1

the initial state of the counter given by PQR as 000, what are the next three states?

2 Components

Component	values	Quantity
Arduino	UNO	1
Jumperwires	M-M	35
Breadboard		2
LED		3
Resistor	220ohms	3
IC	7476	3

Figure.a

3 TruthTable

T	Q	Q'
0	Q	Q'
1	Q'	Q

Truth table for "T" flipflop

4 ExcitationTable

Q	Qn	T
0	0	0
0	1	1
1	0	1
1	1	0

Excitation table of T- flipflop

5 Truthtable(3-stages)

P	Q	R	P+	Q+	R+
0	0	0	0	1	1
0	1	1	1	0	1
1	0	1	0	0	0

Figure :b

6 3stages

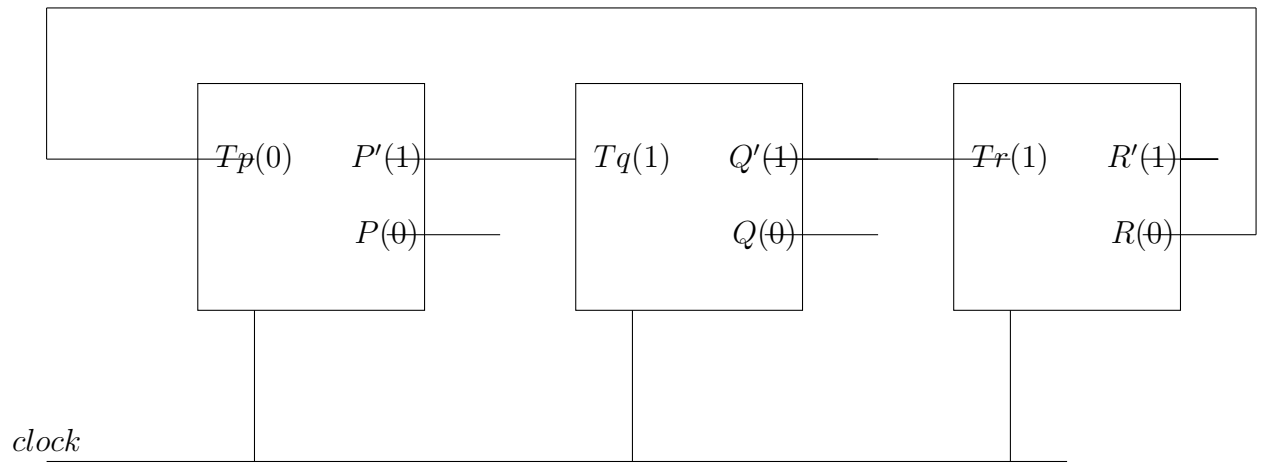


Figure 2

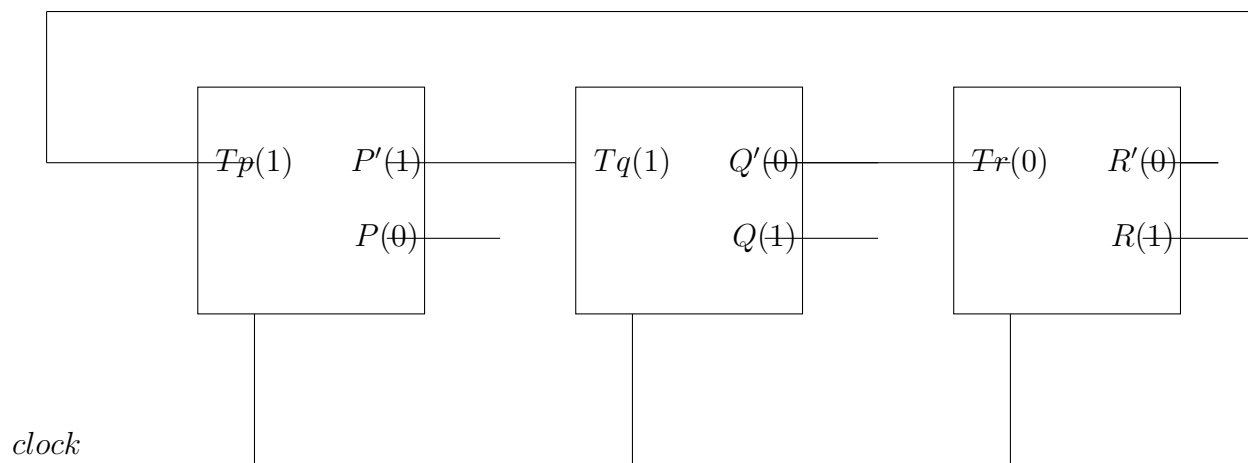


Figure 3


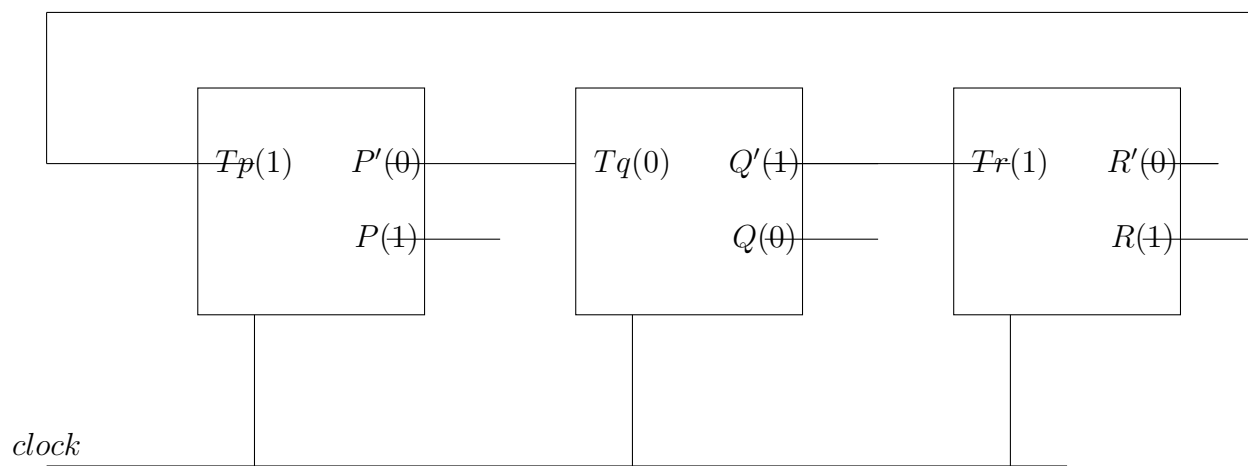


Figure 4

7 Hardware

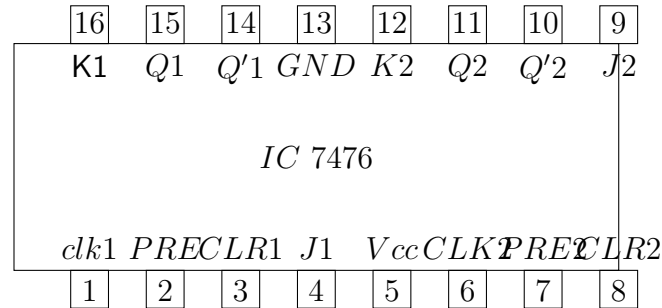The 7476 is a master—slave J-K and the 74LS76 is a negative edge-triggered J-K flip-flop. Both chips have the same pin configuration. Below is the pin diagram of IC7476.



8 Implementation

The connections between Arduino UNO and three IC 7476 is given in below Table

	INPUT			OUTPUT			CLOCK	V _{cc}	GND
ARDUINO	D2	D3	D4	D5	D6	D7	13	5V	GND
7476	16			15			1	5	13

Table 1: connections

9 Procedure

1. Connect the circuit as per the above table.
2. Connect the output pins to the LED's
3. Connect inputs to V_{cc} for logic 1, ground for logic 0
4. Execute the circuit using the below code.

<https://github.com/santhosh-1221/ide/blob/main/code/segment.cpp>

5. Change the values of Q1, Q2, Q3 in the code and verify the truth table